

Experiment 3

S A Aravind Eswar and Eshan Sharma

1 AIM

Study and plot Bode plot of magnitude and phase response for 1-stage, 2-stage, 3-stage RC Low pass filter.

2 MATERIALS AND APPARATUS REQUIRED

- 1) 3 Resistors ($1k\Omega$ used)
- 2) 3 Capacitors ($0.1\mu F$ used)
- 3) Bread Board
- 4) Function Generator
- 5) Oscilloscope

3 THEORY

The transfer function of a 1-stage RC circuit would be the following,

$$\mathbf{H}(s) = \frac{1}{1 + sRC}$$

where,

$$s = j\omega$$

expanding, we get,

$$\mathbf{H}(s) = \frac{1}{\sqrt{1 + (\omega RC)^2}} e^{j\theta}$$

where,

$$\theta = \tan^{-1}(-\omega RC)$$

Applying logarithm on both sides, we get,

$$\begin{aligned} \log \mathbf{H}(s) &= \log \left(\frac{1}{\sqrt{1 + (\omega RC)^2}} e^{j \tan^{-1}(-\omega RC)} \right) \\ &= -\frac{1}{2} \log(1 + (\omega RC)^2) + j \tan^{-1}(-\omega RC) \end{aligned}$$

Calculating Amplitude gain,

$$A = 20 \log (|\mathbf{H}(s)|)$$

$$A = -10 \log \left(1 + (\omega RC)^2 \right)$$

This gives the exact equation for Bode plot of the amplitude gain.

For phase difference,

$$\theta = 20 \tan^{-1} (-\omega RC)$$

Similarly,

The transfer function of 2-stage RC circuit would be,

$$\mathbf{H}(s) = \left(\frac{1}{1 - (\omega RC)^2 + 3sRC} \right)$$

And following this, we get,

$$\log \mathbf{H}(s) = -\frac{1}{2} \log \left((1 - (\omega RC)^2)^2 + (3\omega RC)^2 \right) + j \tan^{-1} \left(\frac{-3\omega RC}{1 - (\omega RC)^2} \right)$$

And,

The transfer function for 3-state RC circuit is given as,

$$\mathbf{H}(s) = \left(\frac{1}{(sRC)^3 + 5(sRC)^2 + 6sRC + 1} \right)$$

And following that we get,

$$\log \mathbf{H}(s) = -\frac{1}{2} \log \left((1 - 5(\omega RC)^2)^2 + (6\omega RC - (\omega RC)^3)^2 \right) + j \tan^{-1} \left(-\omega RC \frac{6 - (\omega RC)^2}{1 - 5(\omega RC)^2} \right)$$

4 PROCEDURE

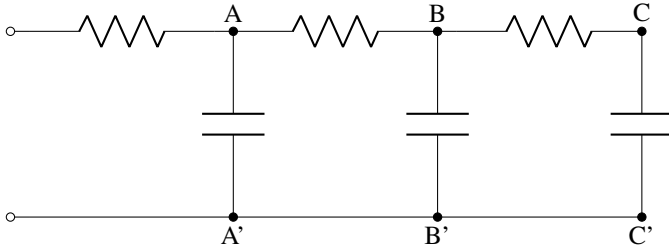


Fig. 1: Circuit Diagram

- 1) Make connections as given in fig. 1

- 2) Give input **V_{in}** in the open end.
- 3) Measure Voltage across $A - A'$ and Phase difference between input voltage and output voltage for 1 cascade circuit analysis.
- 4) Record observations for multiple input frequencies.
- 5) Repeat the experiment for $B - B'$ and $C - C'$ for 2 cascade and 3 cascade circuit analysis respectively.
- 6) Compare the theoreical caltuations and observed values.

5 OBSERVATIONS

f	V_{out}	Δt
10Hz	5.001V	5.6ms
100Hz	5.001V	560 μ s
500Hz	5.001V	300 μ s
1000Hz	3.201V	96 μ s
5000Hz	1.441V	31.2 μ s
10kHz	880mV	18.4 μ s
50kHz	200mV	4.48 μ s
100kHz	104mV	2.2 μ s
500kHz	30mV	—
1MHz	16mV	—

TABLE I: Obsereved 1 Cascade Circuit Response

f	V_{out}	Δt
10Hz	5.001V	5.2ms
50Hz	5.001V	520 μ s
100Hz	5.001V	320 μ s
500Hz	4.401V	216 μ s
1kHz	3.001V	184 μ s
5kHz	580mV	68 μ s
10kHz	184mV	40 μ s
50kHz	16mV	10.8 μ s

TABLE II: Obsereved 2 Cascade Circuit Response

f	V_{out}	Δt
10Hz	4.601V	1.6ms
50Hz	5.001V	200 μ s
100Hz	5.001V	220 μ s
1kHz	3.001V	176 μ s
5kHz	120mV	—
10kHz	30mV	—

TABLE III: Observed 3 Cascade Circuit Response

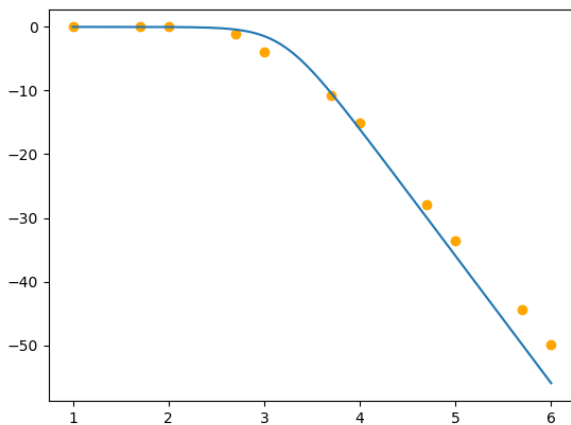


Fig. 2: Amplitude graph for 1 cascade response

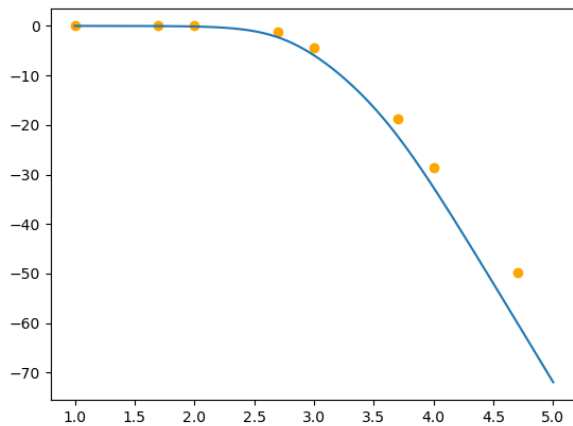


Fig. 3: Amplitude graph for 2 cascase response

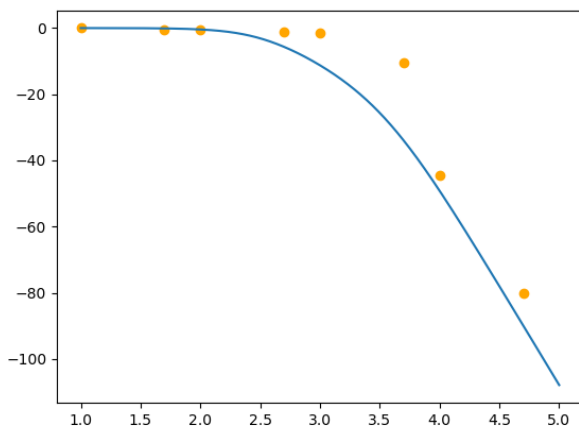


Fig. 4: Amplitude graph for 3 cascase response

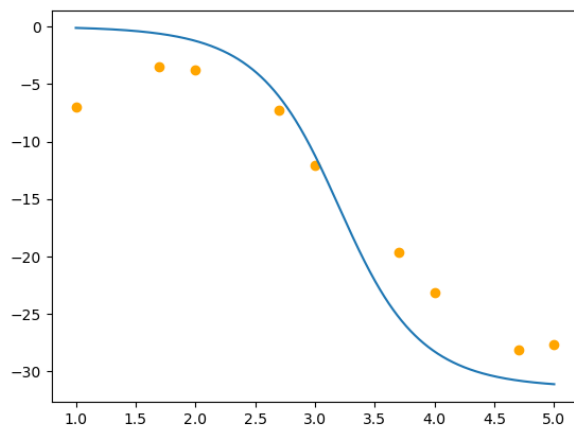


Fig. 5: Phase graph for 1 cascade response

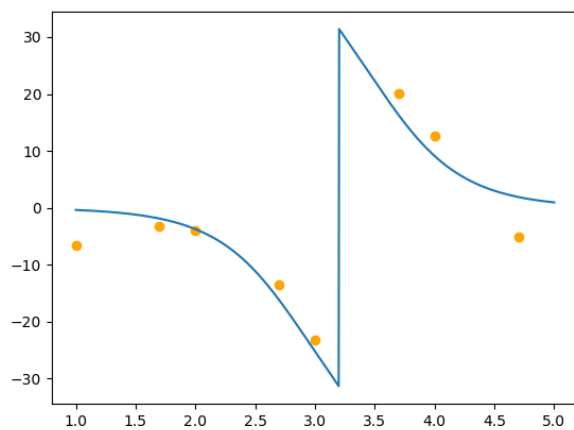


Fig. 6: Phase graph for 2 cascade response

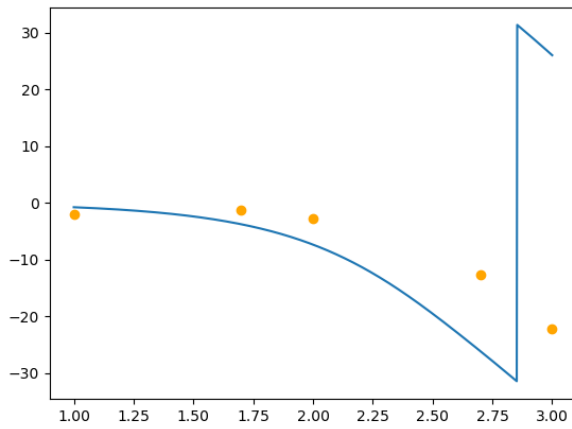


Fig. 7: Phase graph for 2 cascade response