

Experiment 4

S A Aravind Eswar and Eshan Sharma

1 AIM

To study and analyze the transient response of an LC circuit, determine the natural frequency (Ω_n), and calculate the damping ratio (ξ) using theoretical and experimental methods.

2 MATERIALS AND APPARATUS REQUIRED

- 1) 100 μ F Capacitor
- 2) Largest available inductor in the lab (denoted as L)
- 3) Resistor (small value for practical considerations)
- 4) DC Power Supply
- 5) Oscilloscope

3 THEORY

An LC circuit consists of an inductor (L) and a capacitor (C) connected in parallel. When a charged capacitor is connected to an inductor, energy oscillates between the capacitor's electric field and the inductor's magnetic field. This oscillatory behavior is governed by the second-order differential equation:

$$L \frac{d^2 q}{dt^2} + \frac{q}{C} = 0,$$

where $q(t)$ is the charge on the capacitor as a function of time.

The natural frequency of oscillation is given by:

$$\Omega_n = \frac{1}{\sqrt{LC}},$$

where: - L is the inductance in henries (H), - C is the capacitance in farads (F).

For an ideal LC circuit (no resistance), the damping ratio ($\xi = 0$) indicates purely oscillatory behavior. However, in practical circuits, resistance (R) introduces damping, and the damping ratio becomes:

$$\xi = \frac{R}{2} \sqrt{\frac{C}{L}}.$$

3.1 Theoretical Calculations for Given Values

Given:

- Capacitance, $C = 1 \text{ nF} = 1 \times 10^{-9} \text{ F}$,
- Inductance, $L = 2.2 \text{ mH} = 2.2 \times 10^{-3} \text{ H}$,
- Internal resistance of the inductor, $R = 25.2 \Omega$.

3.1.1 Natural Frequency (Ω_n):

$$\Omega_n = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(2.2 \times 10^{-3})(1 \times 10^{-9})}}.$$

Simplifying:

$$\Omega_n = \frac{1}{\sqrt{2.2 \times 10^{-12}}} = \frac{1}{1.483 \times 10^{-6}} \approx 6.74 \times 10^5 \text{ rad/s.}$$

3.1.2 Damping Ratio (ξ):

$$\xi = \frac{R}{2} \sqrt{\frac{C}{L}} = \frac{25.2}{2} \sqrt{\frac{1 \times 10^{-9}}{2.2 \times 10^{-3}}}.$$

Simplifying:

$$\xi = 12.6 \sqrt{\frac{10^{-9}}{2.2 \times 10^{-3}}} = 12.6 \sqrt{4.545 \times 10^{-7}}.$$

Further simplification:

$$\xi = 12.6 \times 6.74 \times 10^{-4} \approx 0.0085.$$

Since $\xi \approx 0.0085$, which is much less than 1, the circuit is **underdamped**, and oscillations will decay over time.

The transient response of the LC circuit can be classified based on the value of ξ :

- 1) **Underdamped** ($0 < \xi < 1$): Oscillations decay over time.
- 2) **Critically damped** ($\xi = 1$): Fastest return to equilibrium without oscillation.
- 3) **Overdamped** ($\xi > 1$): Slow return to equilibrium without oscillation.

The voltage across the capacitor during oscillations can be expressed as:

$$V_C(t) = V_0 e^{-\xi \Omega_n t} \cos(\Omega_d t + \phi),$$

where:

- V_0 is the initial voltage,
- $\Omega_d = \Omega_n \sqrt{1 - \xi^2}$ is the damped natural frequency,
- ϕ is the phase angle.

For experimental analysis, we monitor voltage waveforms using an oscilloscope. The observed oscillation frequency can be compared with theoretical calculations to validate the model.


In summary:

- For a purely LC circuit: $R = 0, \xi = 0, \Omega_d = \Omega_n$.
- For an RLC circuit: $R > 0$, leading to damping and reduced oscillation frequency.

The energy exchange between components can be calculated as:

- Energy stored in capacitor: $E_C = \frac{1}{2} C V_C^2$,
- Energy stored in inductor: $E_L = \frac{1}{2} L I^2$, where $I = -C \frac{dV_C}{dt}$.

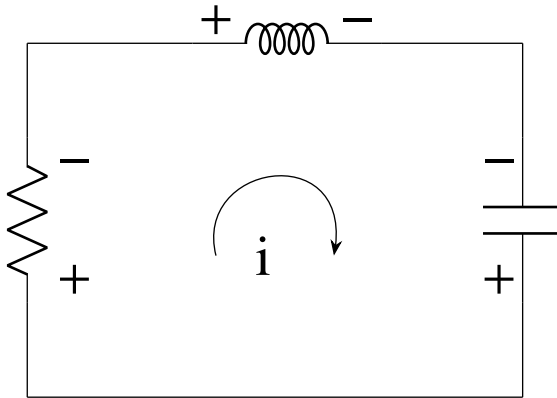These equations form the basis for analyzing transient responses.



4 PROCEDURE

- 1) Precharge the Capacitor:
 - Connect the $100\ \mu\text{F}$ capacitor to a 5V DC power supply.
 - Once charged, disconnect it carefully without discharging.
- 2) Construct the LC Circuit:
 - Connect the charged capacitor in parallel with the largest available inductor.
 - Ensure minimal resistance in wiring.
- 3) Capture Transient Response:
 - Use an oscilloscope to monitor voltage across the capacitor.
 - Observe natural oscillations.
- 4) Calculate Theoretical Values:
 - Compute natural frequency ($\Omega_n = 1/\sqrt{LC}$).
 - Estimate damping ratio ($\xi = R/2\sqrt{\frac{C}{L}}$) if resistance is non-negligible.
- 5) Compare with Experimental Results:
 - Extract oscillation frequency from oscilloscope data.
 - Compare with theoretical calculations.

5 OBSERVATIONS

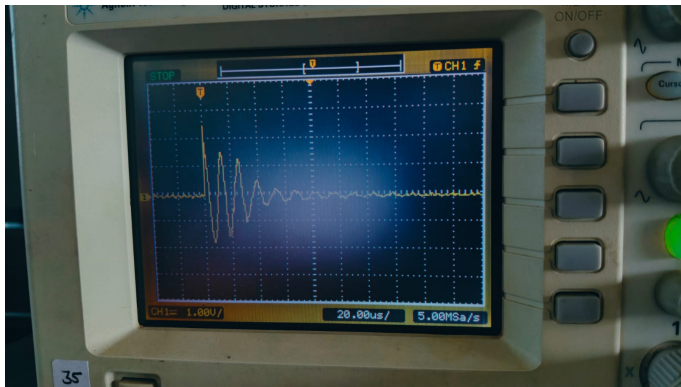


Fig. 1: Transient Response of LC